



FACULTY OF ENGINEERING AND THE ENVIRONMENT

DEPARTMENT OF MINING ENGINEERING

ELECTRICAL ENGINEERING PRINCIPLES

EGS 1206 / EMI 1203 / EMR 1203

Final Examination Paper

July 2022

This examination paper consists of 8 pages

Time Allowed: 3 hours

Total Marks: 100

Examiner's Name: Mr. K. Garapo

INSTRUCTIONS

1. Answer any 5 questions
2. Each question carries 20 **marks** each.
3. Use of calculators is permissible

Additional Requirements

NONE

MARK ALLOCATION

Questions	Marks
Question 1	20
Question 2	20
Question 3	20
Question 4	20
Question 5	20
Question 6	20
Question 7	20
Total Attainable	100

Page 1 of 8

Copyright: Gwanda State University, 2022

Question 1

(a) State Ohm's law and give any one use of a resistor in a circuit. [3]

(b) Given a copper wire of cross-sectional diameter 1 mm and length 1m, calculate its conductance (in siemens), given the resistivity of $1.8 \times 10^{-8} \Omega\text{m}$. [5]

(c) Given the circuit shown in Figure 1, what is the total resistance across the points A and B? [6]

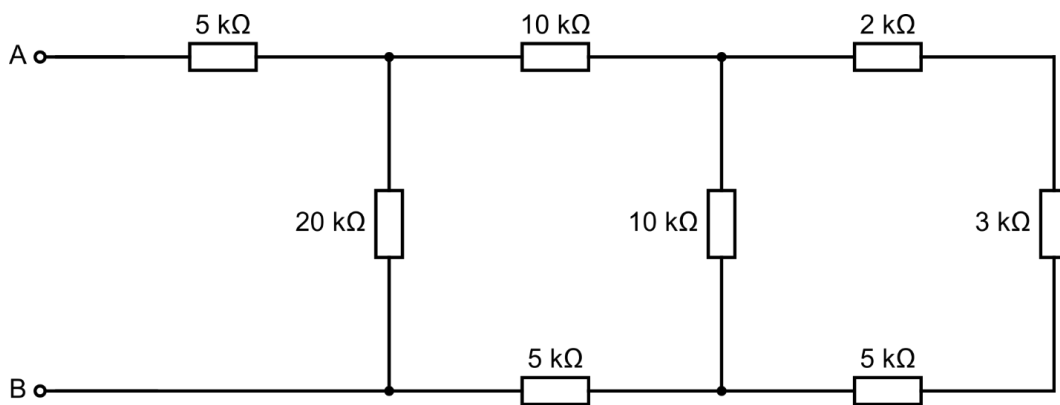


Figure 1

(d) Given the wye and delta circuits shown in Figure 2, calculate the resistances R_a , R_b and R_c , given that $R_1 = 10\Omega$, $R_2 = 15\Omega$ and $R_3 = 5\Omega$. [6]

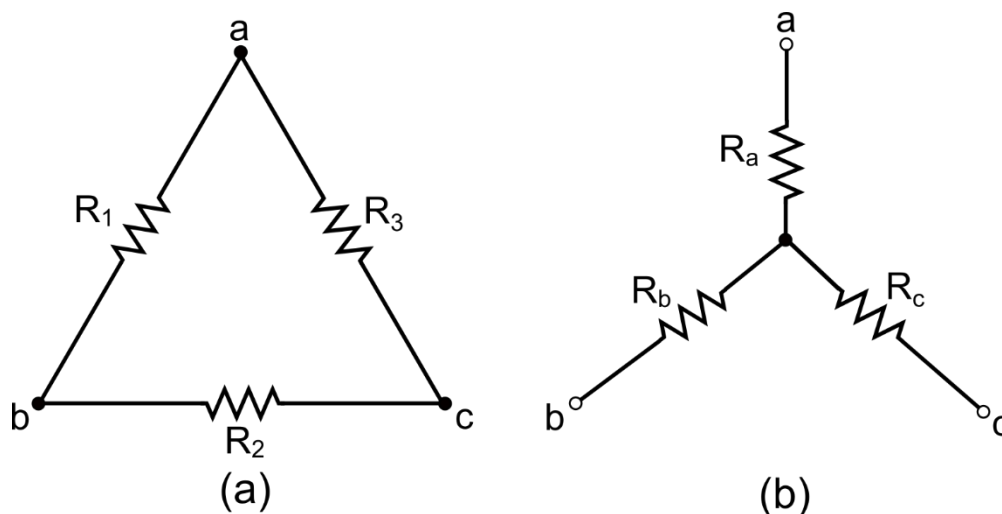


Figure 2

Question 2

(a) Refer to the circuit in shown in Figure 3.

(i) Determine the mesh currents I_1 , I_2 and I_3 . [8]

(ii) What is the current flowing through R_4 ? [2]

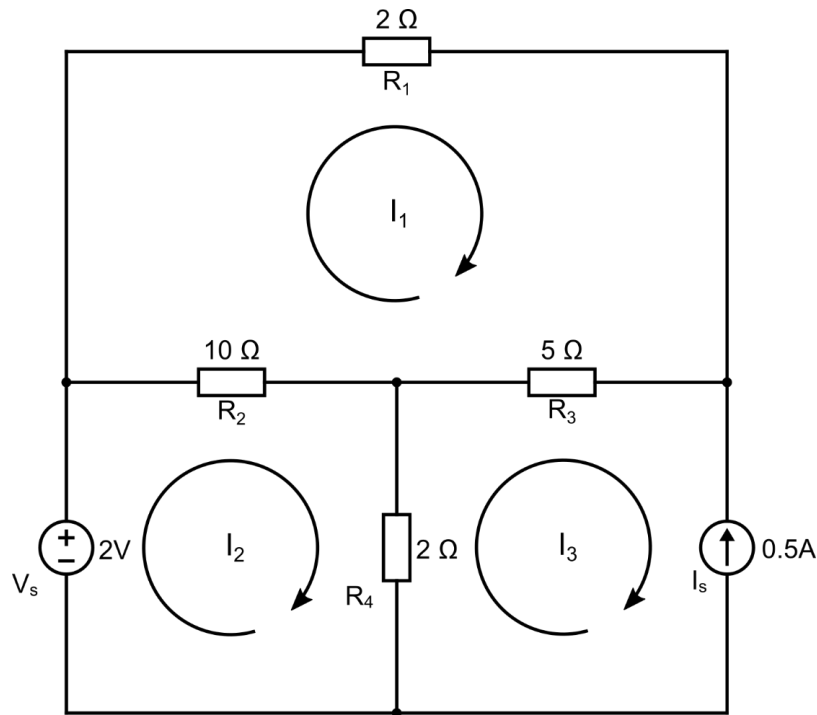


Figure 3

(b) Refer to the circuit shown in Figure 4.

(i) State Kirchhoff's current law (KCL). [2]

(ii) Using Kirchhoff's current law (together with any other applicable circuit laws or theorems), compute branch currents I_1 , I_2 and I_4 , given that $I_3 = 0.27\text{A}$. [8]

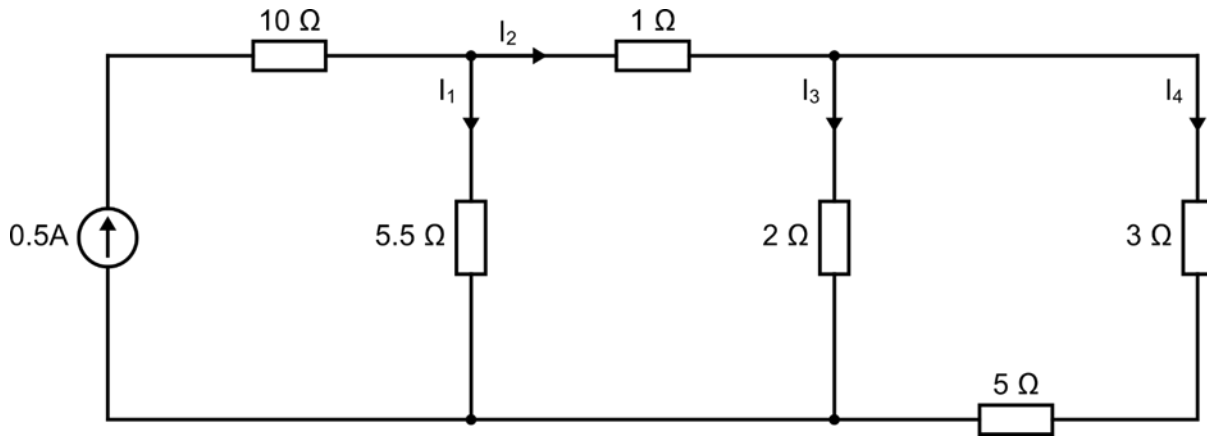


Figure 4

Question 3

Refer to the circuit in Figure 5.

- (a) State Thevenin's theorem. [2]
- (b) For the circuit shown in Figure 5, determine the Thevenin equivalent voltage and resistance. [10]
- (c) Draw the Norton equivalent circuit. [8]

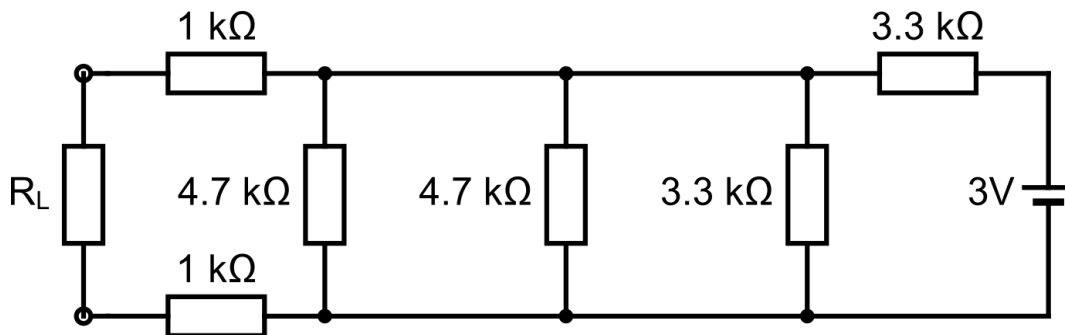


Figure 5

Question 4

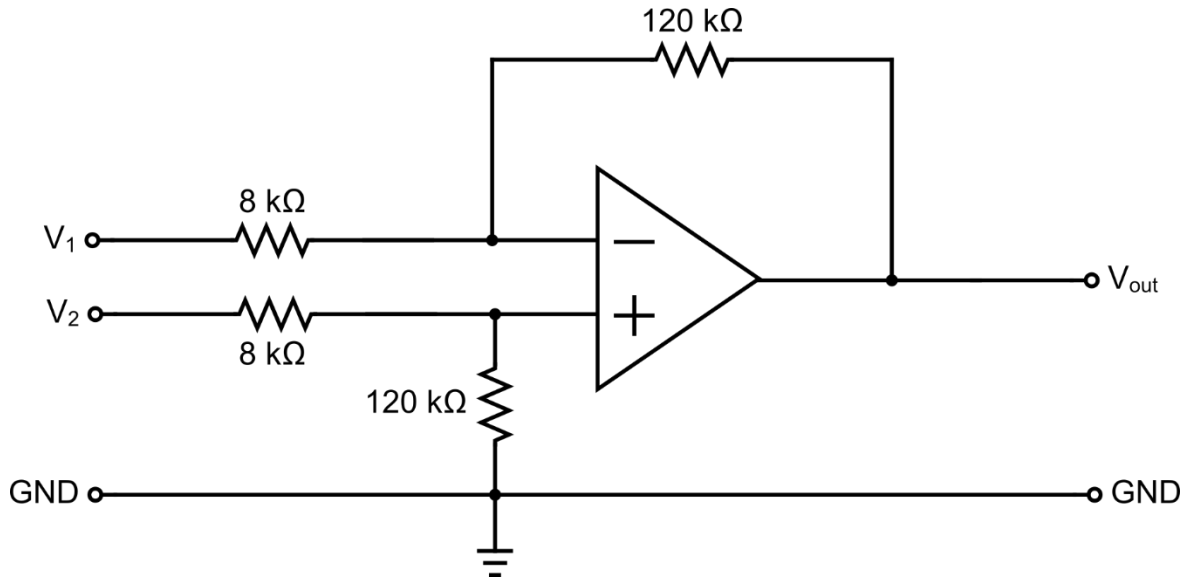


Figure 6

(a) Referring to the differential amplifier in Figure 6, determine the output voltage V_{out} when:

(i) $V_1 = 4 \text{ mV}$ and $V_2 = 0 \text{ mV}$, [2]

(ii) $V_1 = 0 \text{ mV}$ and $V_2 = -6 \text{ mV}$, [2]

(iii) $V_1 = 40 \text{ mV}$ and $V_2 = 30 \text{ mV}$, [2]

(iv) $V_1 = 24 \text{ mV}$ and $V_2 = 42 \text{ mV}$, [2]

(v) $V_1 = -10 \text{ mV}$ and $V_2 = -10 \text{ mV}$. [2]

(b) Referring to the differentiating amplifier in Figure 7, determine the output function V_{out} , given the input function $V_{in} = 5\text{Cos}(\pi t)$, where t is time in seconds. [5]

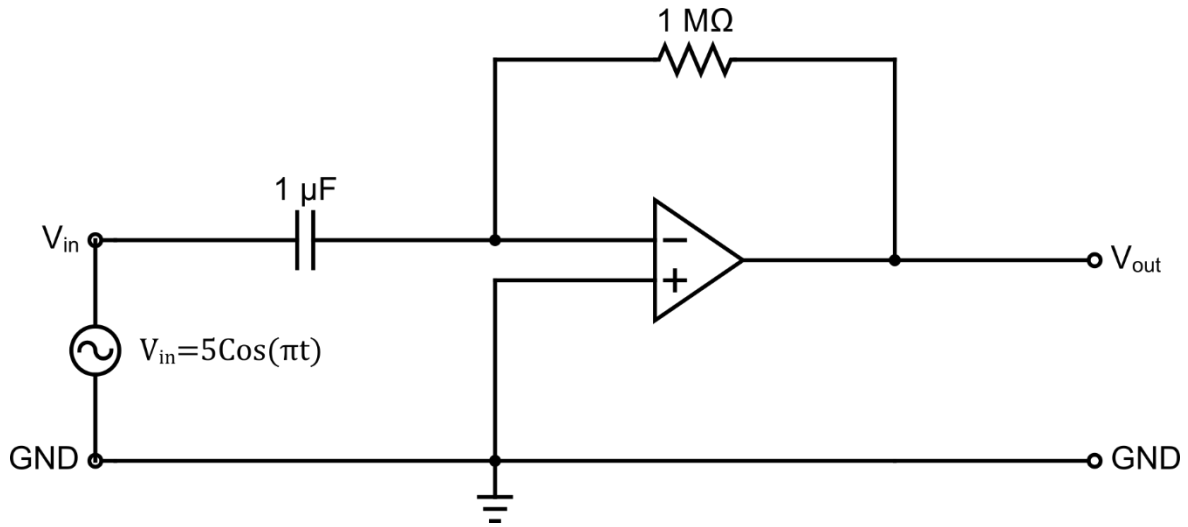


Figure 7

(c) Sketch the output signal V_{out} determined in part (b) as a function of time.

[5]

Question 5

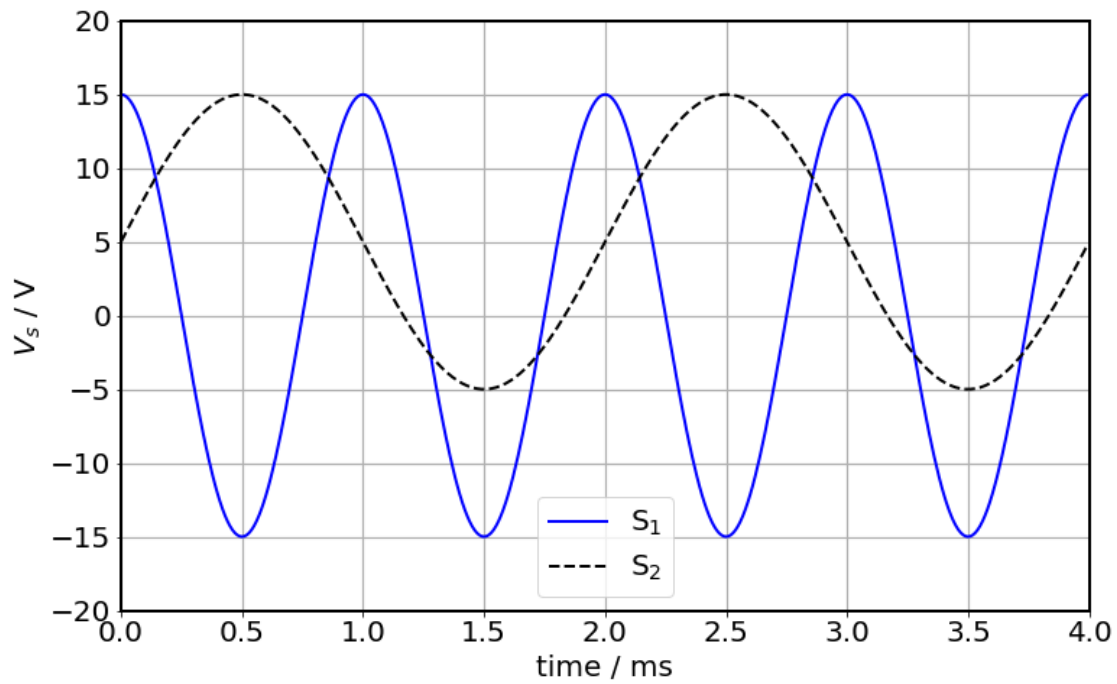


Figure 8

Figure 8 shows the graphs of two alternating voltage signals S_1 and S_2 . For each signal, determine the following:

(a) the d.c. voltage $V_{d.c.}$, [2]

(b) the peak voltage V_p , [2]

(c) the peak to peak voltage V_{pp} , [2]

(d) the r.m.s. voltage V_{rms} , [2]

(e) the period T , [2]

(f) the frequency f , [2]

(g) the function $V = A \cos(2\pi ft + \phi) + V_{d.c.}$, where ϕ is the phase angle, that describes each of the signals. [8]

Question 6

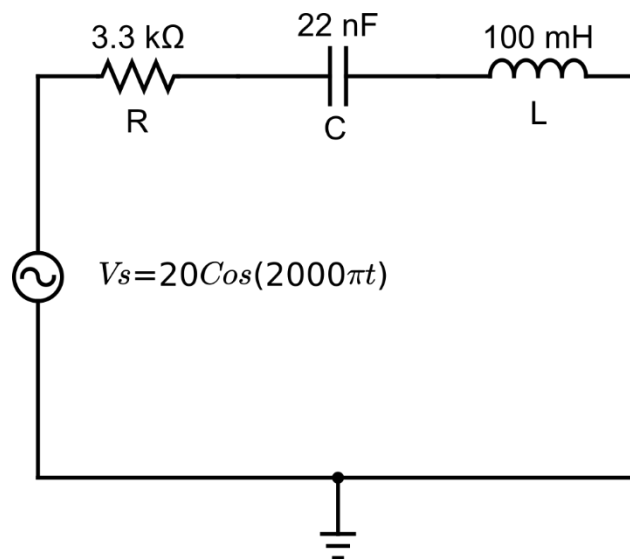


Figure 9

Refer to the circuit in Figure 9.

- (a) What is the capacitive reactance? [3]
- (b) What is the inductive reactance? [2]
- (c) What is the total reactance? [3]
- (d) What is the total impedance of the circuit? [3]
- (e) What is the phase angle between the source voltage and the current? [3]
- (f) What is the voltage across L, C and R? [6]

Question 7

(a) Three inductive loads each of resistance 75Ω and inductance 318.4 mH are connected in delta to a 415 V , 50 Hz , 3-phase supply. Determine

- (i) the phase voltage, [3]
- (ii) the phase current, [6]
- (iii) the line current. [3]

(b) Determine the total power dissipated by three 20Ω resistors when connected to a 440 V , 3-phase supply

- (i) in star, [4]
- (ii) in delta. [4]